

Arduino Workshop

Arduino

see: <http://www.arduino.cc>

Arduino is an open-source physical computing platform based on a simple i/o board, and a development environment for writing Arduino software. Arduino can be used to develop interactive objects, taking inputs from a variety of switches or sensors, and controlling a variety of lights, motors, and other outputs. Arduino projects can be stand-alone, or they can communicate with software running on your computer (e.g. Flash, Processing, MaxMSP). The open-source IDE can be downloaded for free.

- Arduino is an open source project, owned by nobody and supported by many.
- The Team is composed of Massimo Banzi, David Cuartielles, Tom Igoe, Gianluca Martino, David Mellis and Nicholas Zambetti
- Yaniv Steiner and Giorgio Olivero have been supporting the project and are working at using it with the Instant Soup platform.
- The Arduino platform includes the avr-gcc tool chain, uisp, and the Procyon AVR-LIB by Pascal Stang.
- The Arduino language syntax is based on Wiring by Hernando Barragan

Why using Arduino?

- It is flexible, offers a variety of digital and analog inputs, SPI and serial interface and digital and PWM outputs
- It is easy to use, connects to computer via USB and communicates using standard serial protocol, runs in standalone mode and as interface connected to PC/Macintosh computers
- It is inexpensive, around \$30 per board and comes with free authoring software
- It is an open-source project, software/hardware is extremely accessible and very flexible to be customized and extended
- Arduino is backed up by a growing online community, lots of source code is already available and we can share and post our examples for others to use, too!

Sensors

Sensors are electronic devices that measure a physical quality such as light or temperature and convert it to a voltage. This process of changing one form of energy into another is called transduction. Often, sensors are also referred to as transducers.

Sensors can be broadly classified in two categories: **digital** sensors and **analog** sensors. A digital sensor's output can only be in one of two possible states. It is either ON (1) often +5V, or OFF (0), 0V. Most digital sensors work with a threshold. Is the incoming measurement below the threshold, the sensor will output one state, is it above the threshold, the sensor will output the other state.

In contrast to a digital sensor, an analog sensor's output can assume any possible value in a given range. Very often the output of an analog sensor is a variable resistance that can be used to control a voltage. Rather than only being able to toggle between two states (cf. a digital sensor) the analog sensor can output an almost infinite range of values.


In the following examples we will take a look at a couple of digital and analog sensors. We will begin with the simplest digital sensor, the switch. When a switch is open, no current flows. In contrast, when a switch is closed, current flows (i.e. closed = ON). A switch that stays in the position it was put is called a latching switch. Switches can be spring loaded (e.g. microswitches/snap action switches), in this case they are called momentary. A simple switch can be Normally Open (NO) or Normally Closed (NC).



NO - normally open



SPST - single pole, single throw

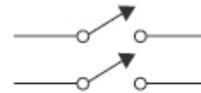

DPST - double pole, single throw



NC - normally closed



SPDT - single pole, double throw



DPDT - double pole, double throw

tactile switch/
pushbutton switch



subminiature switch/
snap action switch



NO NC C


miniature toggle switch



Connecting a Switch to the Arduino Board

This is probably the simplest possible example to get started with Arduino. It uses an external switch and the Arduino board to turn ON or OFF the on-board LED (see: <http://www.arduino.cc/en/Tutorial/Pushbutton>):

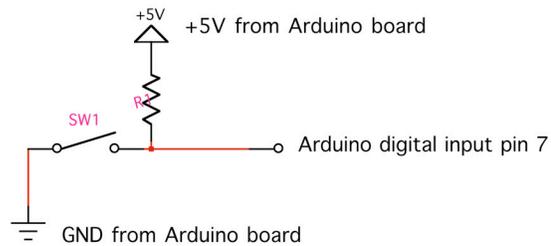1. Connect a switch (you can replace the switch with a plain jumper wire) to the Arduino board in the following way:



R1 = 10k Ω

SW1 can be any type of push button switch or just a wire

Why do we need the resistor R1? R1 guarantees that the Arduino's digital input pin 7 is connected to a constant voltage of +5V whenever the push button is not pressed. If the push button is pressed, the signal on pin 7 drops to ground (GND), at the same time the Arduino's +5V power is connected to GND, we avoid a shorted circuit by limiting the current that can flow from +5V to GND with a resistor (1 - 10 K Ω). Also, if there was no connection from pin 7 to +5V at all, the input pin would be "floating" whenever the pushbutton is not pressed. This means that it is connected neither to GND nor to +5V, picking up electrostatic noise leading to a false triggering of the input.

2. Open the Arduino software and write the following code:

```
/* Basic Digital Read
 * -----
 *
 * turns on and off a light emitting diode(LED) connected to digital
 * pin 13 (onboard LED, when pressing a pushbutton attached to pin 7.
 * It illustrates the concept of Active-Low, which consists in
 * connecting buttons using a 1K to 10K pull-up resistor.
 *
 * Created 1 December 2005
 * copyleft 2005 DojoDave <http://www.0j0.org>
 * http://arduino.berlios.de
 *
 */

int ledPin = 13; // choose the pin for the LED
int inPin = 7;  // choose the input pin (for a pushbutton)
```

```

int val = 0;      // variable for reading the pin status

void setup() {
  pinMode(ledPin, OUTPUT); // declare LED as output
  pinMode(inPin, INPUT);   // declare pushbutton as input
}

void loop(){
  val = digitalRead(inPin); // read input value
  if (val == HIGH) {       // check if the input is HIGH
                           // i.e. button released
    digitalWrite(ledPin, LOW); // turn LED OFF
  } else {
    digitalWrite(ledPin, HIGH); // turn LED ON
  }
}

```

3. Download the code into the Arduino board:
 - a. Select the serial device of the Arduino board from the Tools | Serial Port menu. On the Mac, this should be something with /dev/tty.usbserial in it.
 - b. Compile your code using the “Verify” button in the top left corner of the software window.
 - c. Push the reset button on the board then immediately click the *Upload* button in the environment (don't wait for the board to "come back to life" before pressing the upload button). Wait a few seconds. If successful, the message "Done uploading." will appear in the status bar.
 - d. You are ready to test your first Arduino sensor application.

(For more information on setting up the Arduino see:
<http://www.arduino.cc/en/Guide/MacOSX>, <http://www.arduino.cc/en/Guide/Windows>).

Serial Output

Eventually we would like the Arduino board to send sensor readings to a graphics application on the PC. This can be accomplished by using a communication strategy called “serial communication” to exchange the necessary data. In serial communication, data is transmitted one bit at a time over a single path. In order for the Arduino board and the host computer to understand each other, we need to work with a specific serial data protocol that defines e.g. communication speed (baud rate) and how to begin/end reading data. See chapter 7: “Communicating between Computers” in Dan O’Sullivan Tom Igoe’s book “Physical Computing” for more information on serial communication.

Let's change the above program, so that it also sends a message to the host computer via serial communication in addition to turning the LED on and off:

```
/* Serial Write Basic
 * -----
 *
 * turns on and off a light emitting diode(LED) connected to digital
 * pin 13. The LED will light up when pressing a button. At the same
 * time, Arduino will send two different strings over the serial
 * port depending if the button is pressed or released.
 *
 * Created 1 December 2005
 * copyleft 2005 DojoDave <http://www.0j0.org>
 * http://arduino.berlios.de
 *
 */

int ledPin = 13;    // select the pin for the LED
int buttonPin = 7; // select the pin for the button
int val = 0;       // variable to store the data from the serial port

void setup() {
  pinMode(ledPin,OUTPUT); // declare the LED's pin as output
  pinMode(buttonPin, INPUT); // declare the button pin as input
  Serial.begin(9600);      // connect to the serial port
}


void loop () {
  // read the button and store the value
  val = digitalRead(buttonPin);

  // if the button is at HIGH, turn the LED on, off otherwise
  if (val == HIGH) {
    Serial.print("HIGH");
    digitalWrite(ledPin, HIGH);
  } else {
    Serial.print("LOW");
    digitalWrite(ledPin, LOW);
  }
}
```


Analog Sensors

Analog sensors, such as a photocell often work like a variable resistor the resistance of which is directly influenced by the condition it measures (in the case of the photocell it is the amount of light). Often a voltage divider circuit is used to turn the sensor's changing resistance into a proportional change of voltage that can be understood better by ICs/microcontrollers (such as the Arduino) that you connect the sensor to.

 In the following circuit diagram, a potentiometer is used as a voltage divider, with its slider dividing the overall voltage into two parts R1 and R2. We see that a voltage divider produces a predictable fraction of the input voltage as the output voltage.




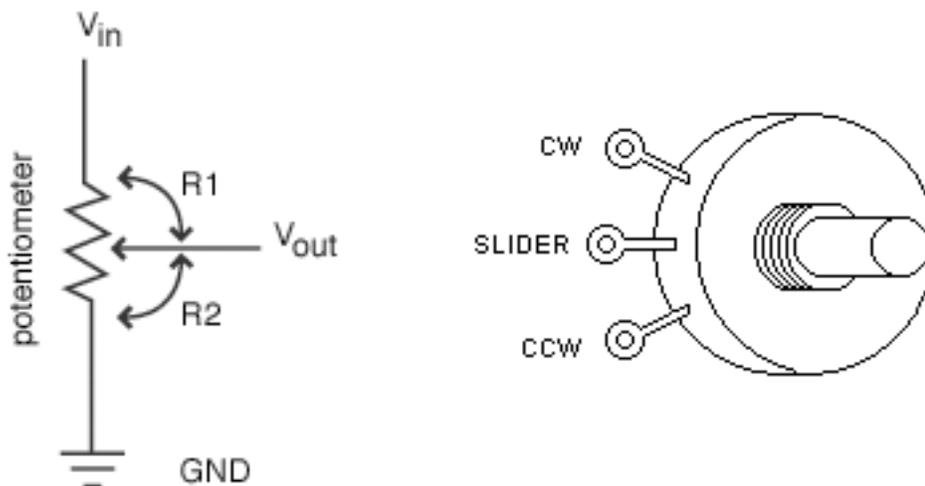This general description of a voltage divider is related to the potentiometer as follows:





Connecting a Potentiometer to the Arduino Board

 In this example we would like to connect a potentiometer to the Arduino and control the brightness of an external LED by turning the potentiometer's knob. The Arduino board uses pulse width modulation (PWM) to dim the LED. In effect, the digital output is pulsed rapidly (turning the LED ON and OFF many times per second) to create the impression of the LED being evenly dimmed.



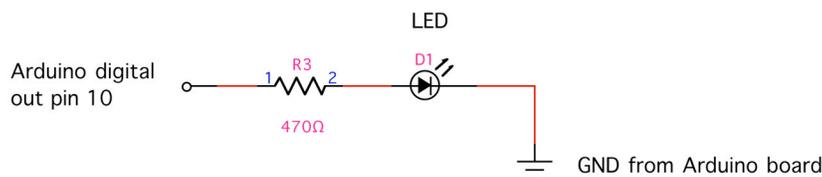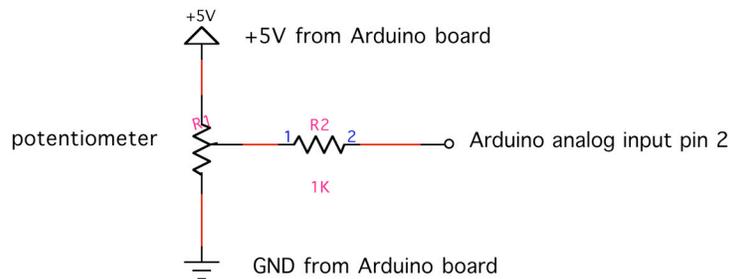1. Build the following two simple circuits and connect them to the Arduino board:



2. Write the following code and upload it onto the board:

```
/* Analog Read Send
 * -----
 *
 * turns on and off a light emitting diode(LED) connected to digital
 * pin 13. The amount of time the LED will be on and off depends on
 * the value obtained by analogRead(). In the easiest case we connect
 * a potentiometer to analog pin 2. Sends the data back to a computer
 * over the serial port.
 *
 * Created 24 January 2007
 * copyleft 2007 Fabian Winkler
 *
 */

int potPin = 2;    // select the input pin for the potentiometer
int ledPin = 10;   // select the pin for the LED
int val = 0;       // variable to store the value coming
                  //from the sensor
int pwmVal = 0;   // variable for PWM output



void setup() {
  pinMode(ledPin, OUTPUT); // declare the ledPin as an OUTPUT
  Serial.begin(9600);      // use the serial port to send the values
  back to the computer
}

void loop() {
  val = analogRead(potPin); // read the value from the sensor
  Serial.println(val);      // print the value to the serial port
  pwmVal = val/4;          // PWM is 8bit (0-255), analog in is 10bit
                          // (0-1023), so we need to convert

  analogWrite(ledPin, pwmVal);
}
```

Connecting a Photocell to the Arduino Board

 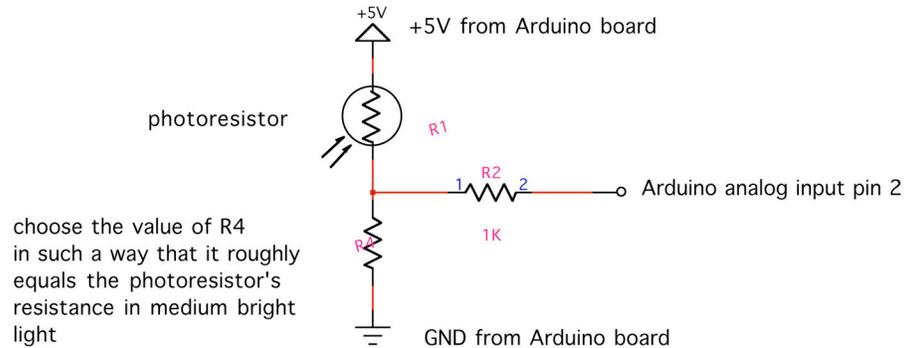This example shows you how to read a photocell (photoresistor) with the Arduino. The code is analog to the example above.



Sensors with PWM output

Some more advanced sensors, such as the MEMSIC2125 dual axis accelerometer sensor use a different way to output sensor values, which is neither a straight ON or OFF signal, nor is it a variable voltage range. The output of these sensors is pulse width modulated (see page 8 above). The width (i.e. timing) of the pulses that the sensor sends out can be easily measured with the Arduino board's `pulseIn` function (see: <http://www.arduino.cc/en/Reference/PulseIn>).



MEMSIC2125 dual axis accelerometer

Appendix

Signal conditioning

What to do when the voltage range that a sensor provides and the range of an Arduino's input pin don't match up? The following is a tutorial from Acroname Robotics and can be found online at:

<http://www.acroname.com/robotics/info/articles/interface/interface.html>

Contents

- Introduction
- Dividing Voltages
- Amplifying Voltages
- Shifting Voltages
- Combining Conversions
- Conversion Impurities
- Power Supply Ideas
- Further Reading

Introduction


The interface of various sensors to a controller like the Arduino typically involves either conditioning or converting voltage levels into the range the controller requires. Many systems use A/D converters to make the sensor value relevant in a program or data logging configuration. These converters have a fixed range of voltages they can convert from with 0–5V being by far the most common.

Sensors often create voltages in different ranges than those required by the controllers they are being interfaced to which requires the conversion of one voltage to another. This conversion often breaks down into a combination one or more of three types, amplification, dividing, and shifting.


Dividing Voltages

Voltage dividing is probably the easiest transformation you can perform on sensor outputs to alter the value being connected to a microcontroller or other circuit.

The mathematical equivalent of what you are trying to achieve when dividing voltages is a simple division. For instance, say you have a sensor that outputs 0–100V and you want to convert this to 0–5V for interface to the A/D input on your Arduino. The goal would be to create a 20:1 ratio of voltage which means dividing the original sensor output voltage by a factor of 20. So we need a small circuit that will accomplish the following graphically:

 

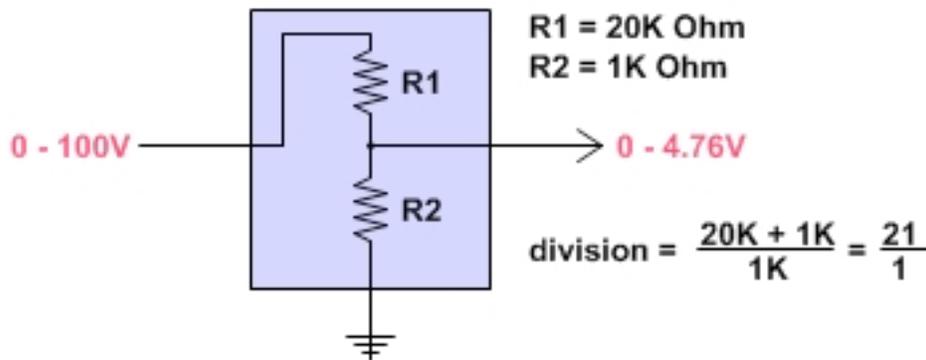The easiest way to accomplish this division is using a few resistors to form a voltage divider. The resistors are wired up in series to create intermediate voltages based with the desired division. The above example could be accomplished as follows:




This voltage divider uses the input as the top of the resistor ladder and ground as the bottom. The actual division is defined by the proportion of resistance between the two resistors.

Notice the above circuit does not work out to an exact division by 20. This is because the resistors used are commonly found resistor values. Precision resistors with exact tolerances can be used but are often not needed since the original output of sensors typically varies. Here the resulting output voltage is slightly below the maximum of 5V but with a reasonable A/D converter like the 10-bit converters used in the Arduino board would still offer plenty of dynamic range in the sensor readings.


Amplifying Voltages

Voltage amplification is required for a class of sensors that create small voltages. Often sensors of this type are converting some sort of physical energy such as acceleration, temperature, or other minimal physical force into a voltage. This conversion is often an inefficient conversion and the measured energy is minimal which results in very small voltages generated by the sensor. To make these small voltages meaningful, they must be amplified to a usable level.

The equation for amplification is the exact opposite of dividing. You want to multiply the output voltage from a sensor to gain the full range of your A/D input or other interfaced circuit. Lets say you have an accelerometer which measures accelerations in g (gravity) units. A sensor like this may have a response of 312mV/g which means the sensor will generate 0.312V for each gravity unit of force it encounters. Now, say you would like to measure up to 2 gravity units (2g) with your detector with the full range of your 0-5V A/D converter. This means you need to multiply the output voltage of your accelerometer by a factor of about 16 to get the desired range and sensitivity in your measurements. So we want to accomplish the following graphically:

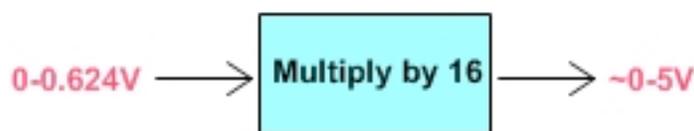

Probably the most common way to multiply a voltage is using an amplifier. Here, we will use a common Operational Amplifier (Op Amp) to multiply the voltage. These Op Amp circuits are extremely common in electronics and there are volumes devoted specifically to the various characteristics and performance of each. We use one of the original versions which is widely available and easy to interface called the 741. Here is one circuit that will amplify the voltage by a factor of about 16:

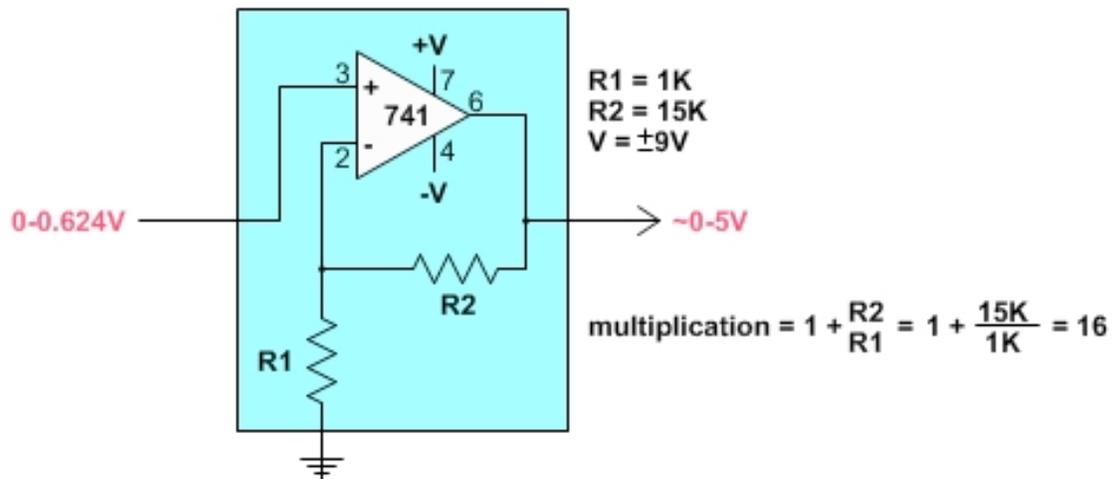


There are some things to note about this circuit. Again, changing resistance values gives a different voltage amplification (multiplication). The small numbers indicate the pins of the 741 package that you would connect to for this circuit (it is an 8 pin chip). Also, notice the additional power supply which is both positive and negative. This is very common for Op Amp circuits. Since the Op Amp is powered by a plus/minus voltage of 9V, the absolute output can at best be 9V. In practice, the output voltage will probably be slightly less.

The gain for this amplifier may not be exactly linear, depending on the input and output voltages. This can often be hidden in the noise of the sensor and accuracy of the A/D conversion on the other end but it should be considered. The higher the gain of an amplifier, the larger the margin of error and noise.

Shifting Voltages


Shifting voltages can be a requirement for sensor data that are generated symmetrically about a common (often ground) voltage. A simple example of this would be a motor acting as a generator where spinning in one direction creates a positive voltage and spinning in the other direction creates a negative voltage. Since most common A/D converters in microcontrollers deal with a 0-Vcc range for conversions, sensors that are symmetric about the ground voltage reference need to be shifted into the 0-Vcc range.

 The equation for shifting is then the addition or subtraction of an offset from the original sensor's voltage. For example, if your sensor produces -2 to 2V, you would want to add 2V to the output for reading with a common 0-5V A/D converter. This addition would result in a final output of 0-4V which the A/D converter could then use. This conversion looks like this graphically:



This circuit is a two-stage summing amplifier using an Op-Amp chip (the 1458) that houses two op-amps on a single chip. Notice there are some fixed values of resistors that essentially create a voltage summing circuit. The input on one side is a resistor network that creates a fixed voltage to sum with the input voltage. The variable resistor values change this resistor network's set voltage. You could substitute a potentiometer for R1 and R2 to make the addition variable, by twisting the potentiometer.

 
The addition circuit also requires a plus/minus 9V power supply for the op-amps. In addition, a tap from the 5V supply used for the logic is used although this could be done with the positive 9V side as well, provided the voltages are computed correctly.



Combining Conversions

So the above conversions define addition, subtraction, multiplication, and division of a voltage. Each of these conversions can be thought of in isolation as shown above or they can be combined to create composite conversions. We essentially have an algebra of blocks we can use to achieve a wide variety of overall conversions.

 Say you have a sensor that creates -100 to 100V and you want to read the value with a 0-5V A/D converter. You would need to scale down the original voltage to -2.5 to 2.5V first and then offset the result by adding 2.5V to get the result into the desired range of 0-5V for your A/D converter. You can chain together the conversions for such an effect which would look like this graphically:




Conversion Impurities

The above conversions all introduce impurities in the resulting signal in the form of noise, non-linearity, and other corruptions of the original input voltage. Care must be taken to minimize the number of stages and also to order them for reduced error. Testing and careful thought can typically reduce these impurities to a minimum but they cannot be disregarded.

There is a general rule of thumb with regard to these introduced impurities. The more you are changing the original voltage, the more impurities you will introduce. For instance, an amplification of 100x would be generally noisier than one of 2x.

Power Supply Ideas

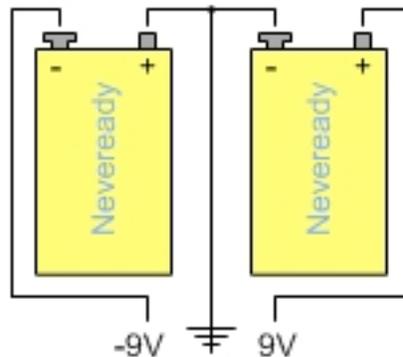Several of these circuits require a plus/minus 9V supply for the Op Amps. This can readily be accomplished using two standard 9V batteries. More sophisticated options include standard power supplies, charge pumps and inverters and several other options. The 9V battery is cheap, simple and it works well. Op Amp circuits tend to be pretty efficient so the batteries should last quite some time.



Circuit Diagram of $\pm 9V$ Battery Supply

Further Reading

The subject of sensor interfaces is vast. This article attempts to give some basics that are easy, practical, and quick to implement. Here are two great references to consider:

- * The Art of Electronics, by Horowitz and Hill
- * Op Amp IC Circuits, by Forrest M. Mims III